

High Frequency Basics

**Tom Strouth
GigaTest Labs, Inc.**

Guest Speaker and Author:

Tom Strouth


GigaTest Labs, Inc.
7337 Bollinger Road
Cupertino, CA 95014
(408) 996-7500

Current Activities:


Owner and operator of GigaTest Labs, Inc.. Tom provides as a service, electronic network measurements at microwave frequencies, on semiconductors, hybrids, packages, interconnect structures, components and systems. Certified network measurement equipment with a frequency range from 45 MHz to 40 GHz and results are verified.

Brief Synopsis of Background:

Applied Physics, University of Missouri at Rolla ('63-'65), University of Missouri at St. Louis ('69-'71). Instrumental in establishing Microwave Integrated Circuit and GaAs FET technologies at Teledyne MEC ('71-'80). Served as Manufacturing Manager at Harris Microwave Semiconductor ('80-'87) and made significant contributions to the growing GaAs device business. He established Strouth Technical Sales in 1987, representing leading edge manufactures of semiconductor technology, and GigaTest Labs in 1989, providing measurement services for the electronics industry.

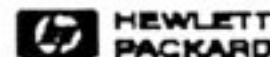

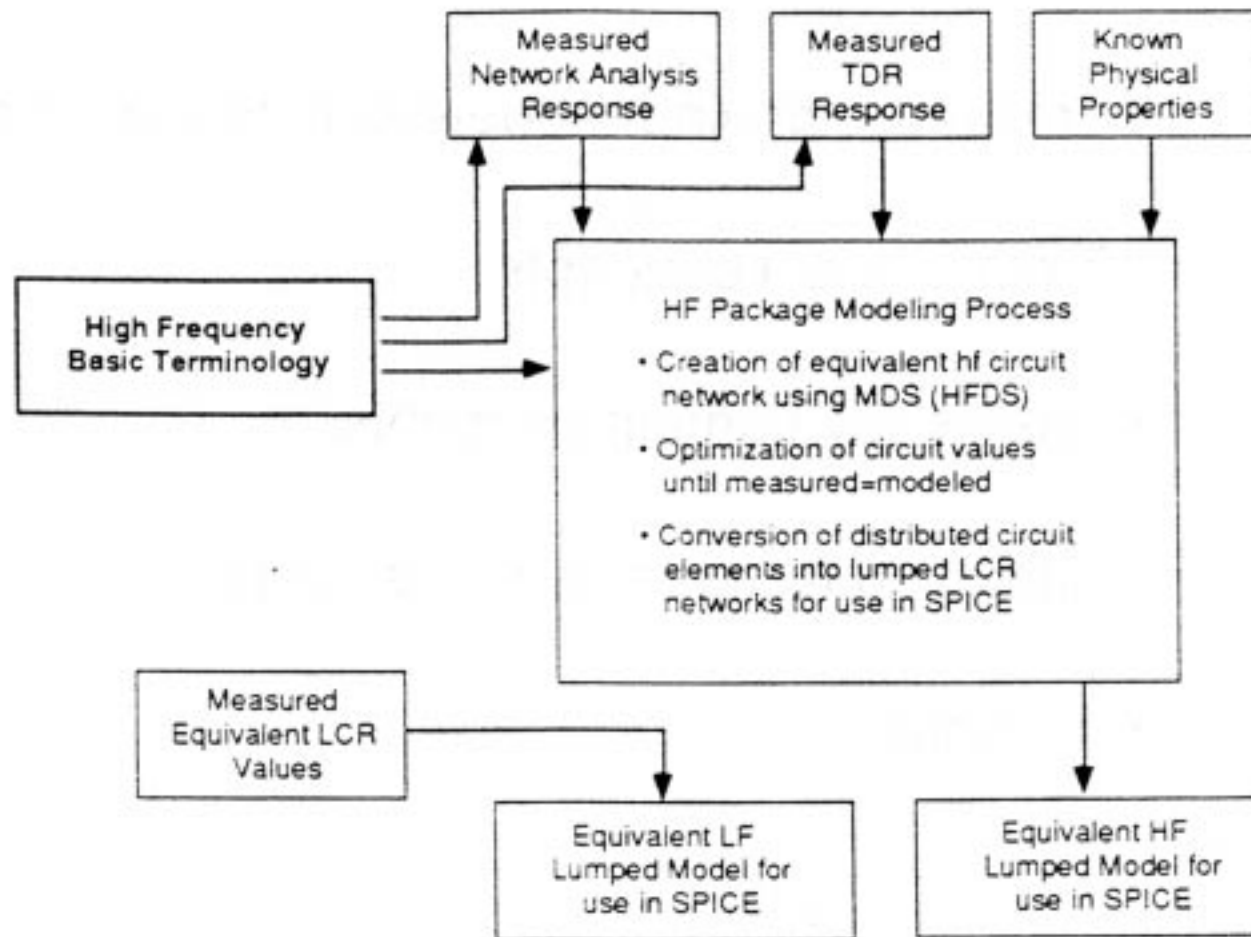Package Characterization and Modeling Process



Outline

- Transmission line models and construction
- Time domain concepts
- Frequency domain concepts
- Time and frequency relationships
- Summary




Transmission Line Models and Construction

- Transmission line models
- Transmission line construction
- Impedance curves
- Transmission line crosstalk model



Simple Transmission Line Models

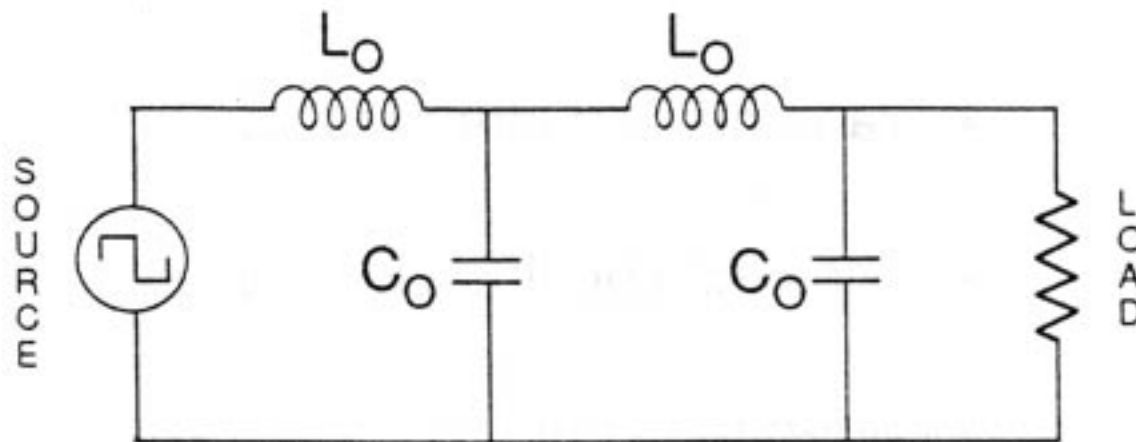

$$L_0 = \frac{\text{Inductance}}{\text{Unit Length}}$$


$$C_0 = \frac{\text{Capacitance}}{\text{Unit Length}}$$

Transmission
Line Impedance

$$Z_0 = \sqrt{\frac{L_0}{C_0}}$$



Transmission Line Model

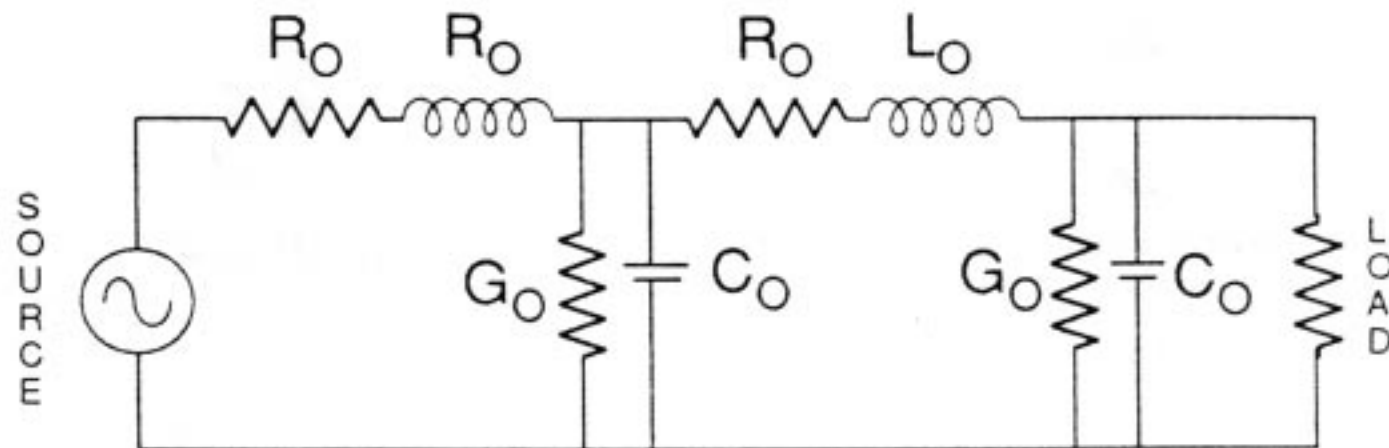

$$L_O = \frac{\text{Inductance}}{\text{Unit Length}}$$

$$G_O = \frac{\text{Conductance}}{\text{Unit Length}}$$

$$C_O = \frac{\text{Capacitance}}{\text{Unit Length}}$$

$$R_O = \frac{\text{Resistance}}{\text{Unit Length}}$$

Transmission
Line Impedance

$$Z_O = \sqrt{\frac{R_O + j\omega L_O}{G_O + j\omega C_O}}$$




1900 Transmission Lines




Two-Wire Line



Coaxial Line

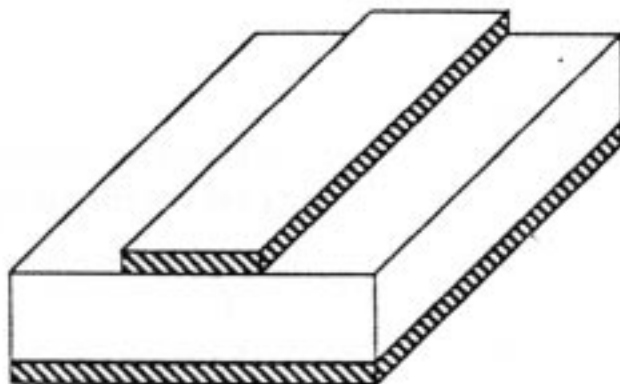


Microstrip Line


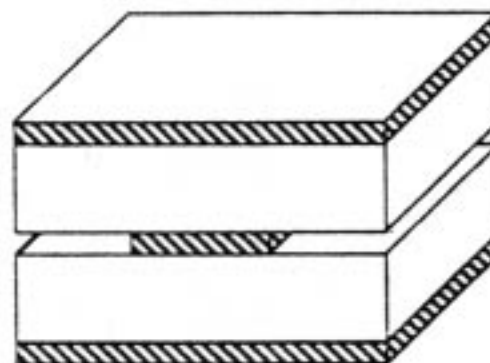


Strip Line


Typical Transmission Line Structures

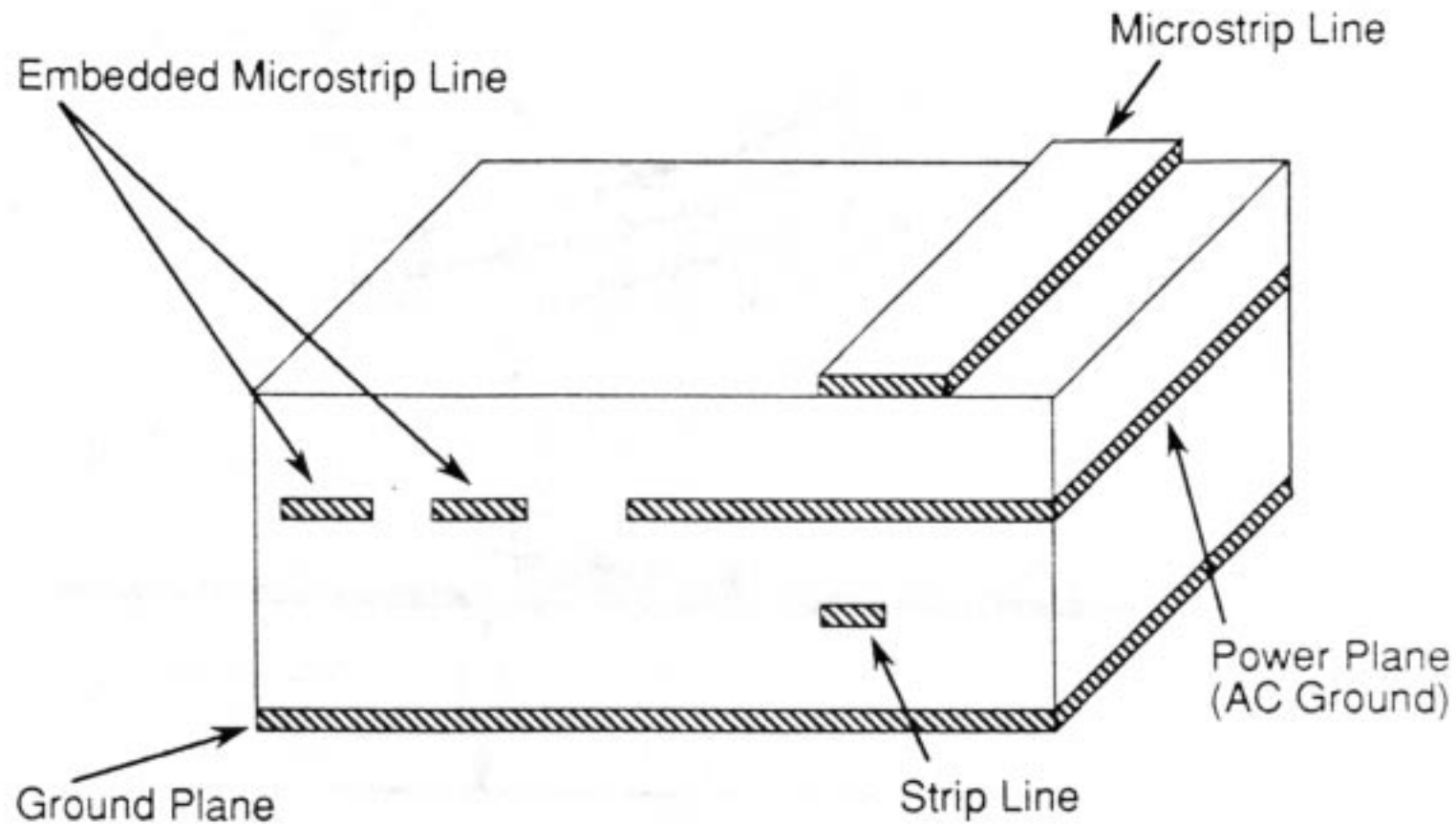

Microstrip Impedance Curves

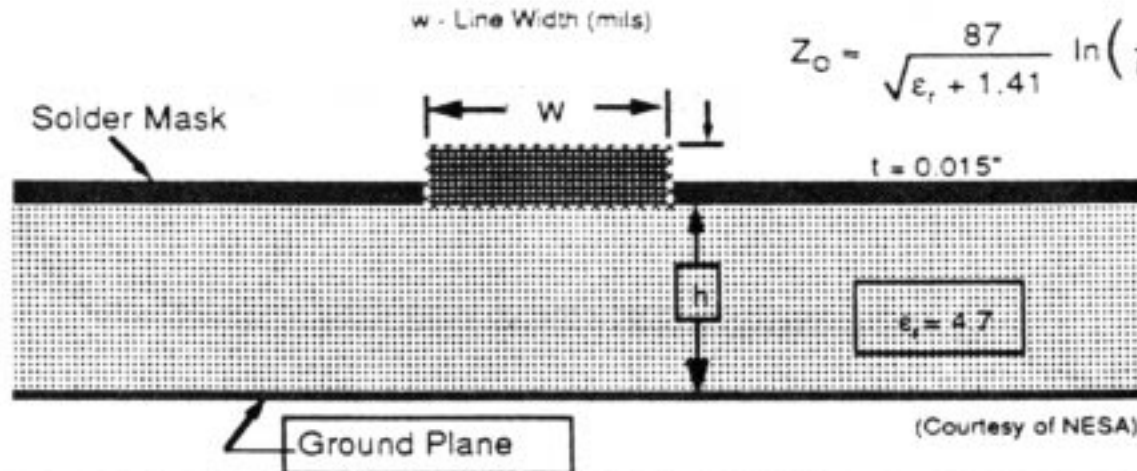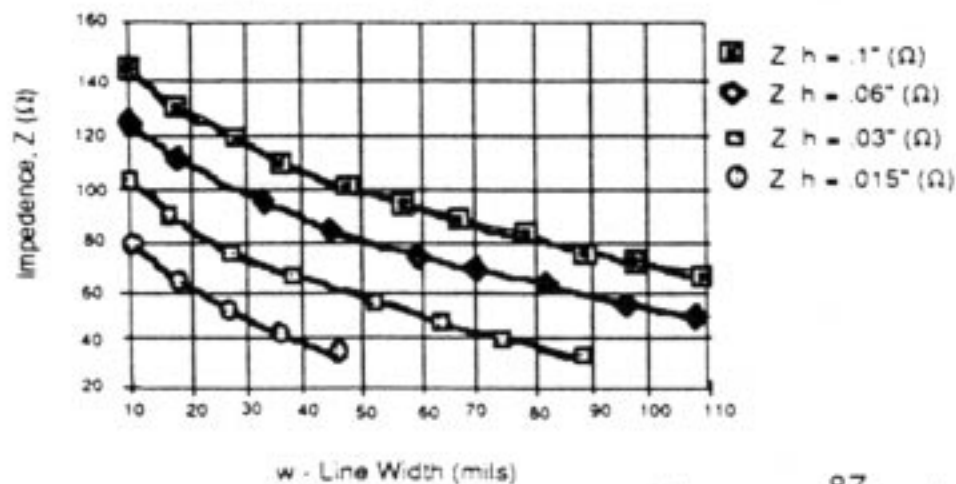

Transmission Line Crosstalk Model

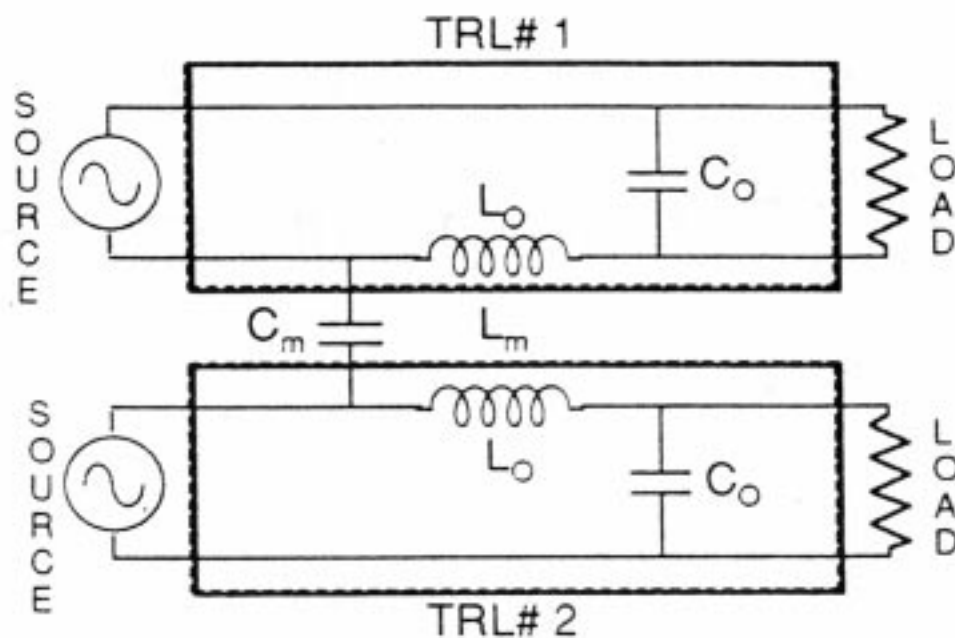

COUPLING COEFFICIENTS, K_f and K_b


$$K_f = -\frac{1}{2} \left[\frac{L_m}{Z_o} - C_m Z_o \right] \quad K_b = -\frac{1}{4TD} \left[\frac{L_m}{Z_o} + C_m Z_o \right]$$

Time Domain Concepts

- TDR - Time domain reflection
- TDT - Time domain transmission
- Examples



Time Domain Reflection (TDR)

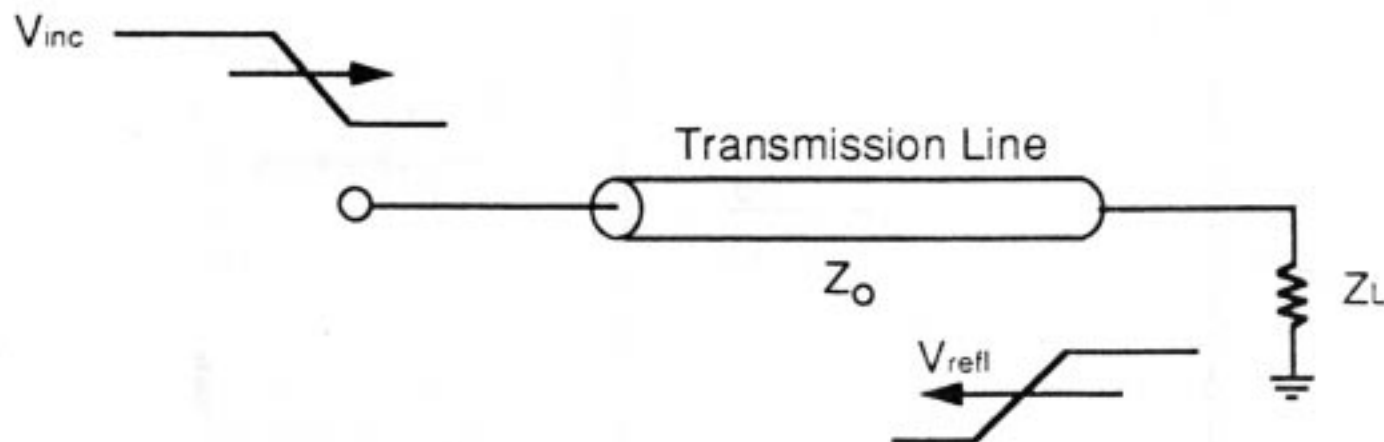


$$V_{refl} = \frac{Z_L - Z_o}{Z_L + Z_o} V_{inc}$$

$$\text{Where } \Gamma = \frac{Z_L - Z_o}{Z_L + Z_o}$$

$\rho = |\Gamma| = \text{Reflection Coefficient}$

$$V_{refl} = \rho * V_{inc}$$

TDR - Important Conditions


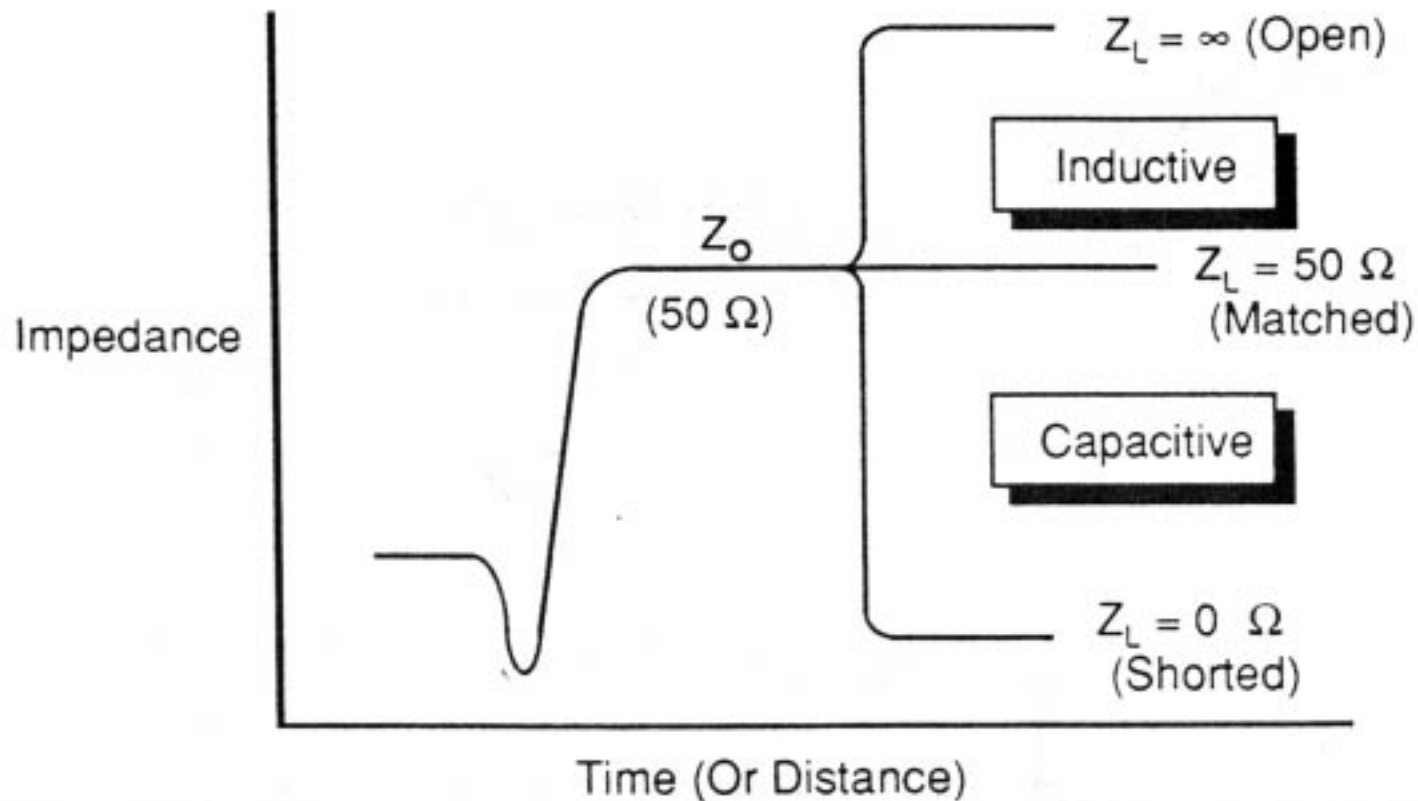


$Z_L = Z_o$ is called an "impedance match"

$Z_L \neq Z_o$ is called an "impedance mismatch"



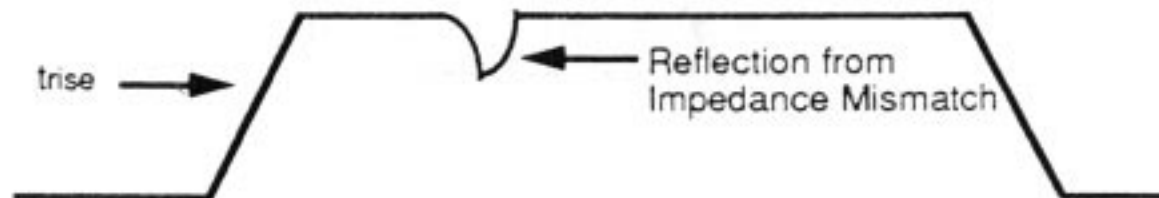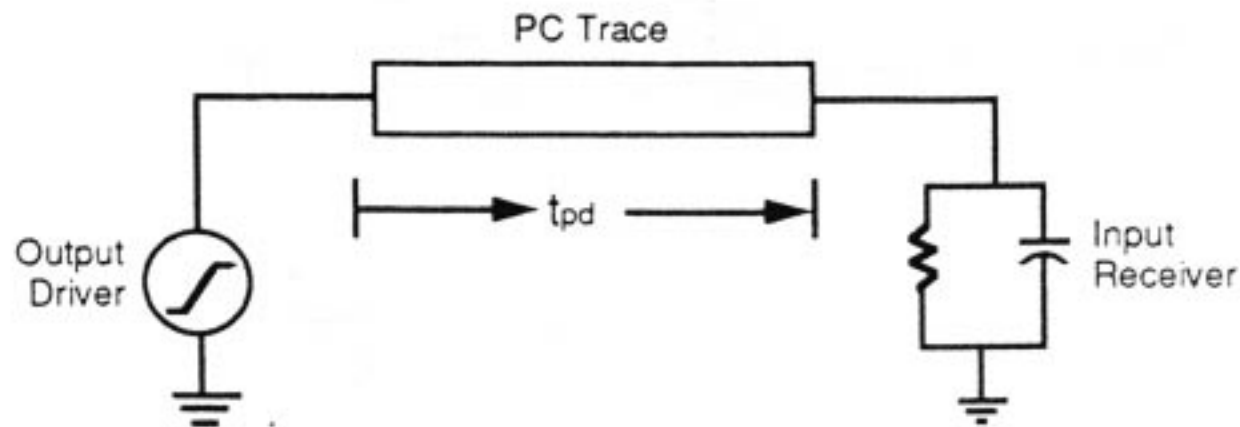When Does Impedance Mismatch Cause Problems?




$$t_{rise} < 2t_{pd}$$

$$t_{pd} \approx 1.017 (0.475 \epsilon_r + 0.67)^{1/2} \text{ ns/ft}$$



Time Domain Transmission (TDT)

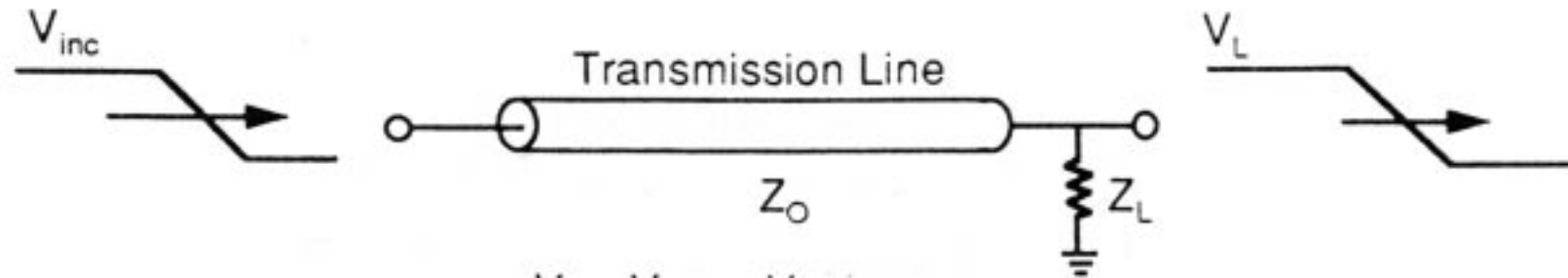


$$\begin{aligned} V_L &= V_{inc} + V_{refl} \\ &= V_{inc} + V_{inc} \frac{Z_L - Z_0}{Z_L + Z_0} \end{aligned}$$

$$V_L = (1 + p)V_{inc}$$


Where

$\tau = (1 + p)$ = Transmission Coefficient


TDT - Important Information

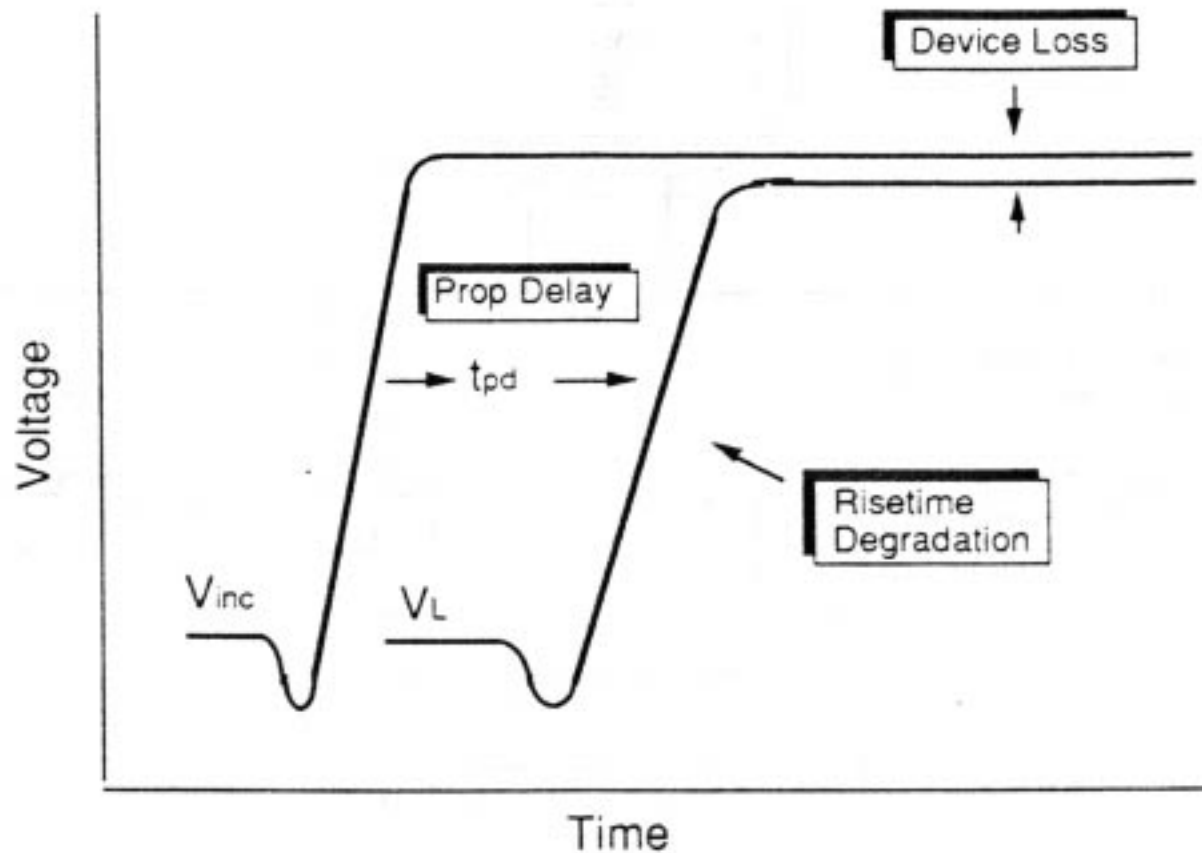

Example Package Measurement

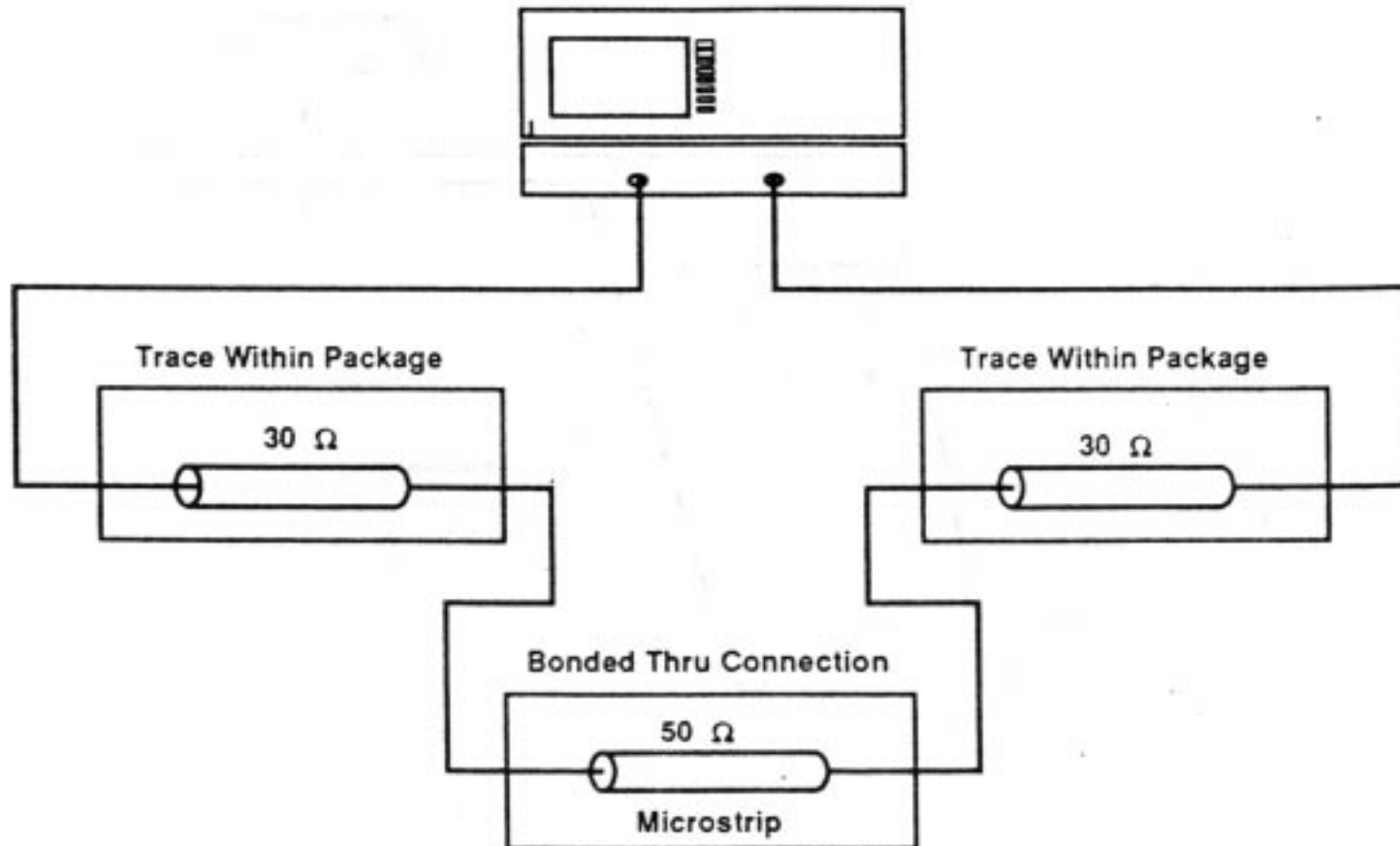

TDR Measurement Example

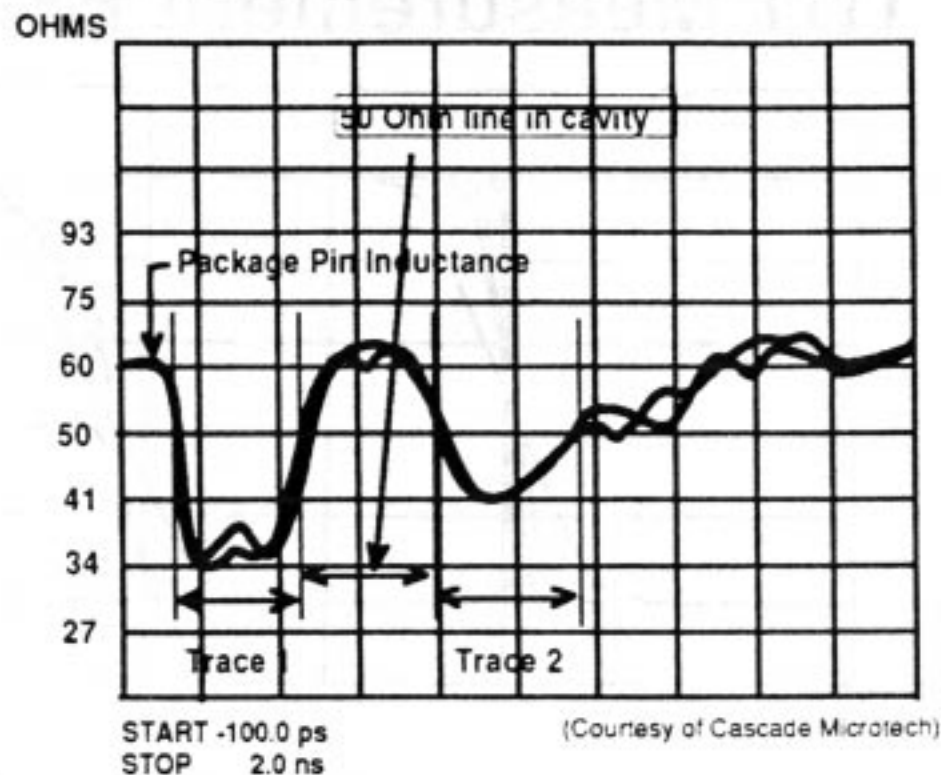


Observations:

- Mismatch between traces and 50 Ω line dominant factor
- Package pin inductance negligible
- Can gain insights into general circuit topology for SPICE from observing TDR of package



TDT Measurement Example

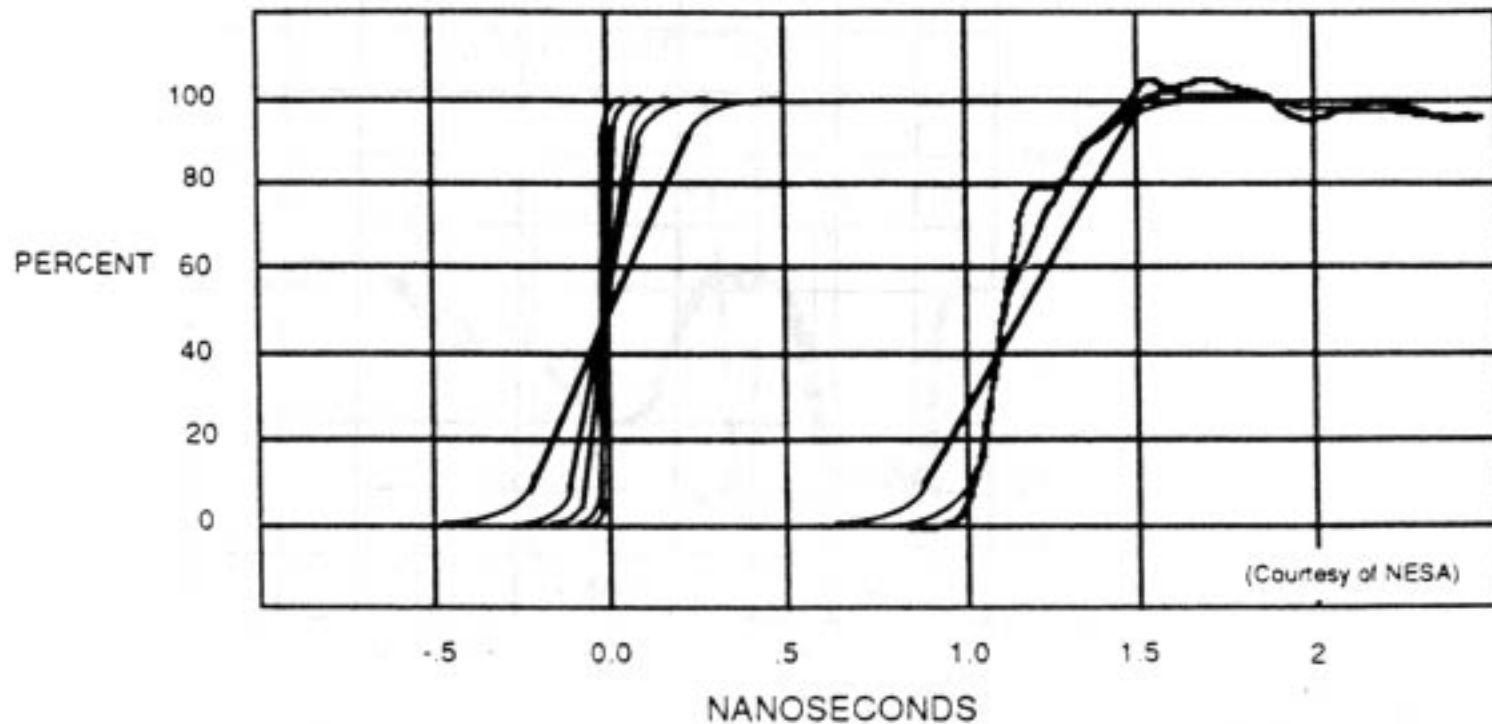

Observations:

- Propagation delay through package is about 1.2 ns
- Loss through package is negligible
- Risetime degradation is about 200 ps




Frequency Domain Concepts

- S_{11} and S_{22} - Reflection parameters
- S_{21} and S_{12} - Transmission parameters
- Measurement examples



High Speed (Microwave) Concepts

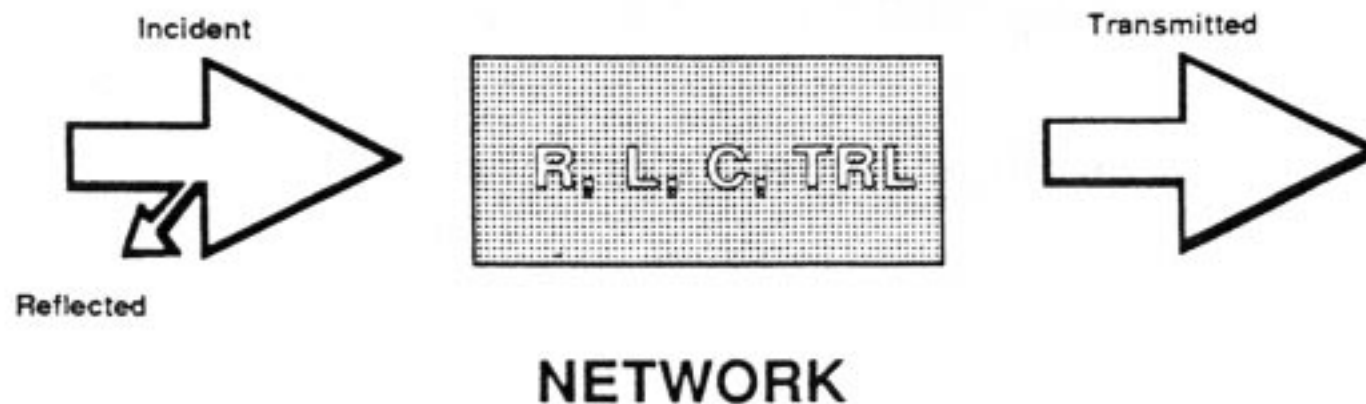

Reflection Parameters

$$\Gamma = \frac{V_{\text{Reflected}}}{V_{\text{Incident}}} = \frac{Z_L - Z_0}{Z_L + Z_0} \quad \text{Reflection Coefficient}$$

Return Loss

S - Parameters

S_{11}, S_{22}

VSWR


Impedance

$$\rho = |\Gamma|$$

TDR



S_{11} and S_{22} Important Conditions

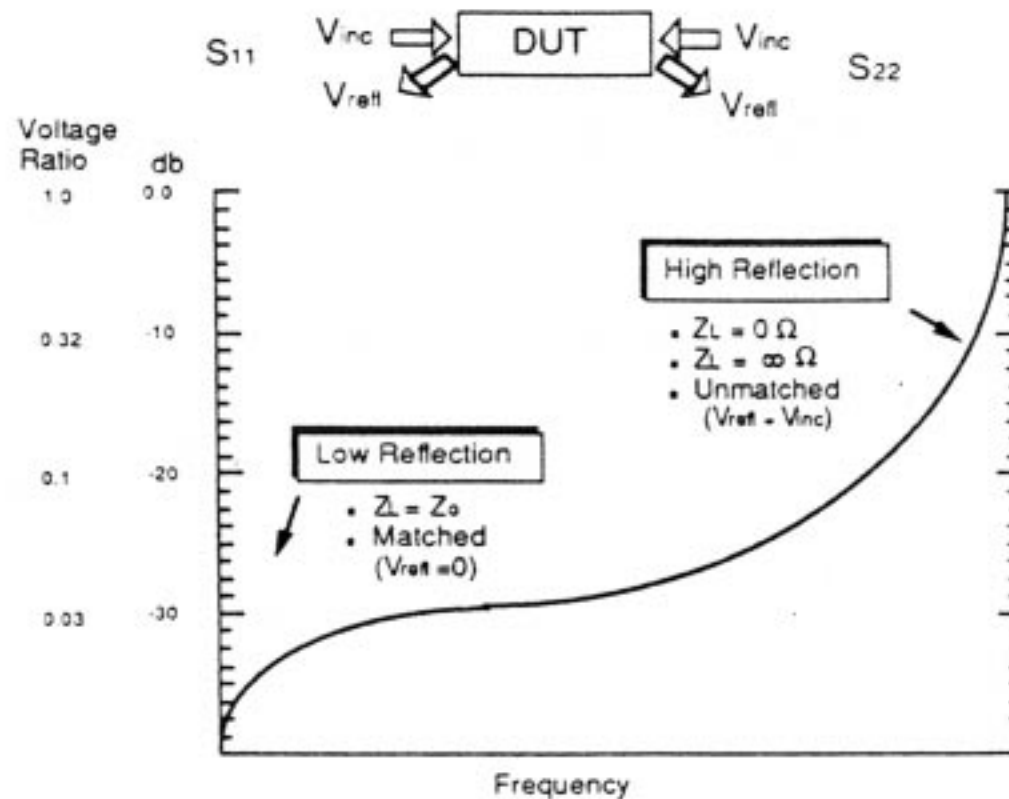

$$S_{11} = S_{22} = \frac{V_{refl}}{V_{inc}}$$



Transmission Parameters

$$T = \frac{V_{\text{Load}}}{V_{\text{Incident}}} = \frac{2Z_L}{Z_L + Z_0} \quad \text{Group Delay}$$

Gain/Loss

S - Parameters

S_{11}, S_{22}

Transmission
Coefficient


Insertion Phase

$$\tau = |T|$$


TDT



S_{21} and S_{12} Important Conditions

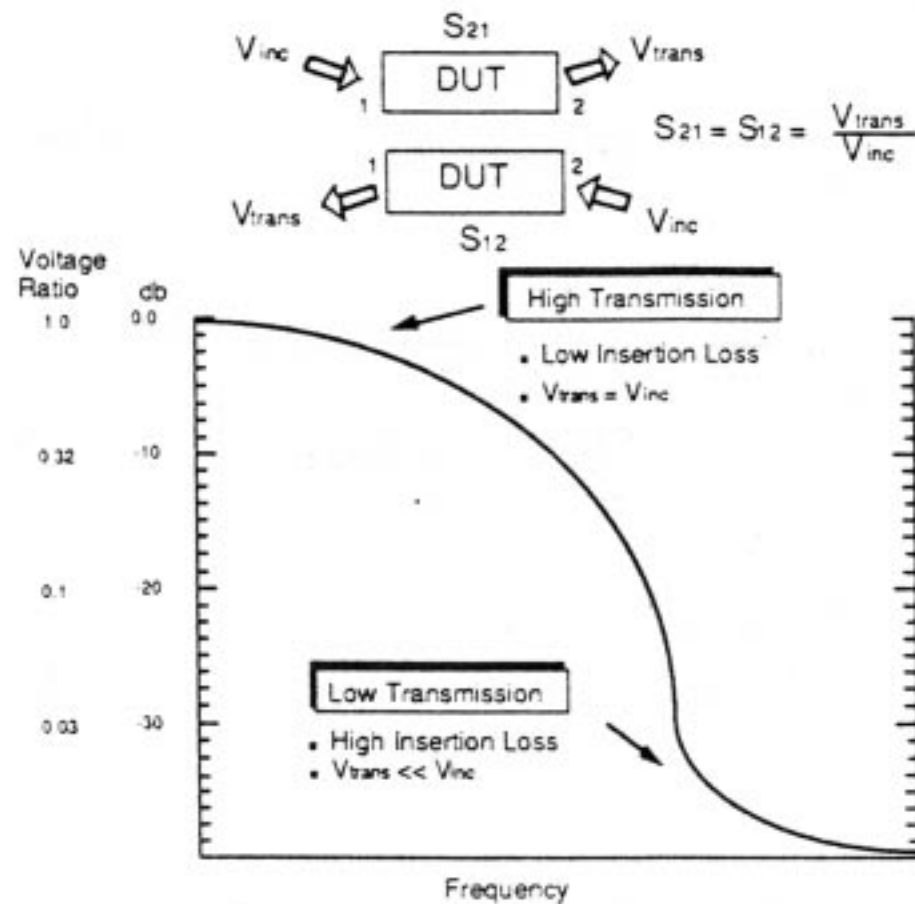



Scattering Parameters

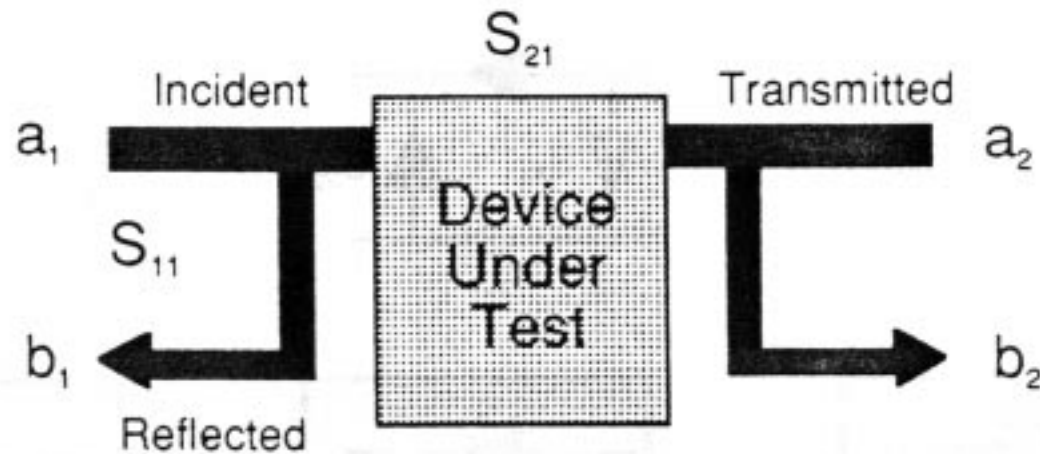

$$S_{11} = \frac{\text{Reflected}}{\text{Incident}} = \frac{b_1}{a_1}$$


$$S_{21} = \frac{\text{Transmitted}}{\text{Incident}} = \frac{b_2}{a_1}$$

Scattering Parameters

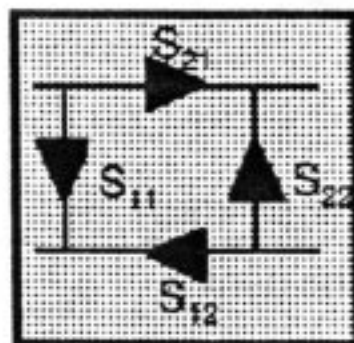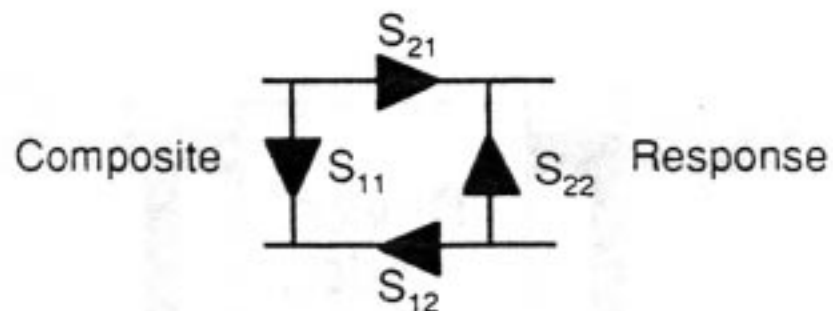


Interconnect

+

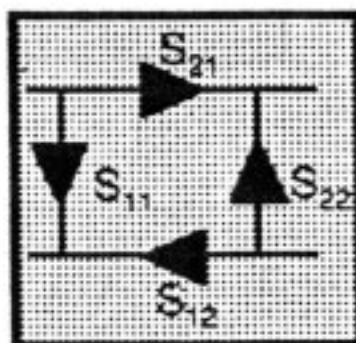


PC Board

+

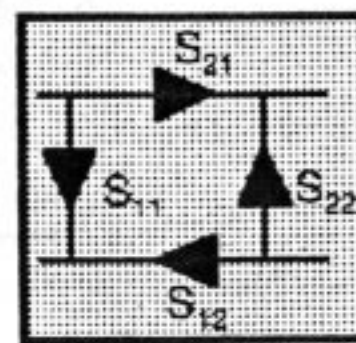


Package/Device

Example Package Measurement

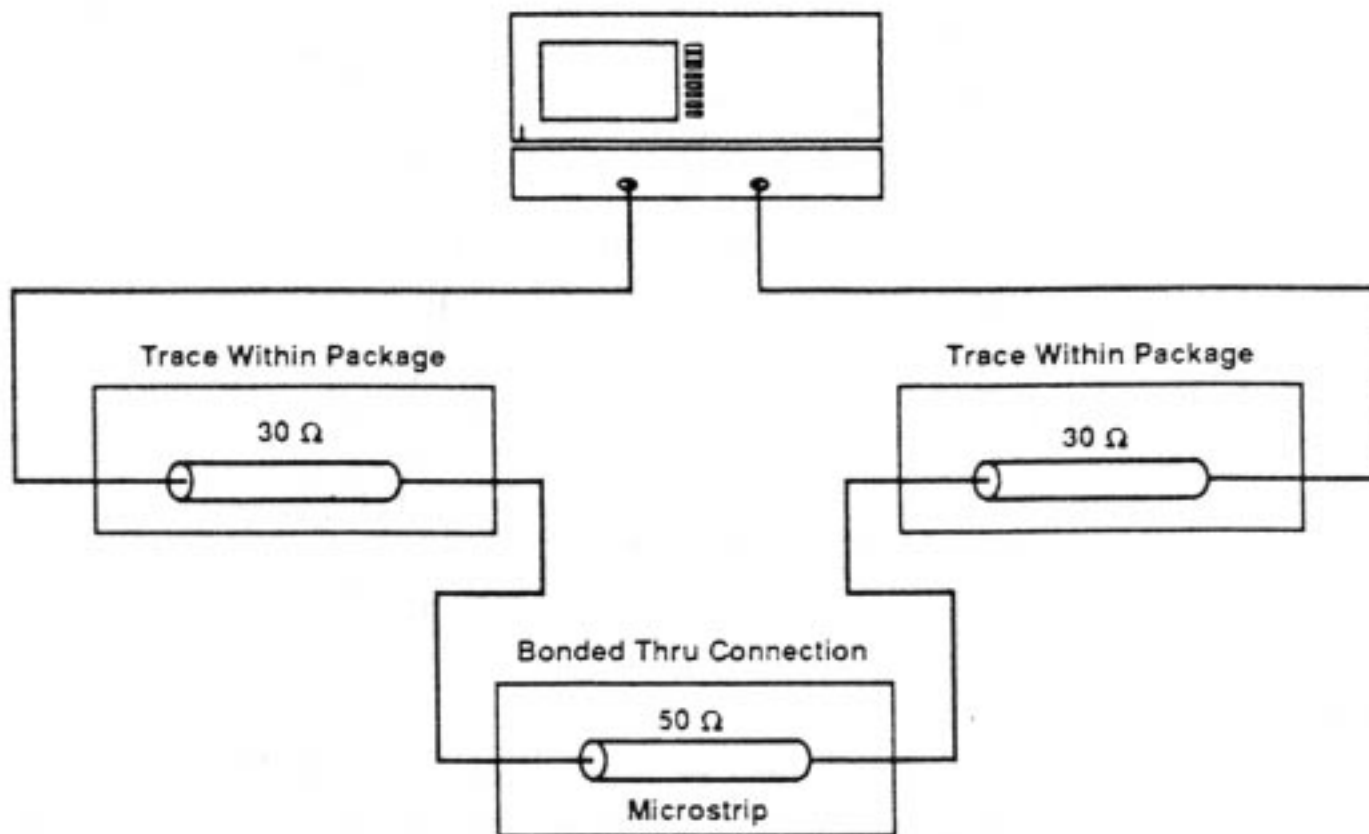


S_{11} and S_{21} Measurement Example

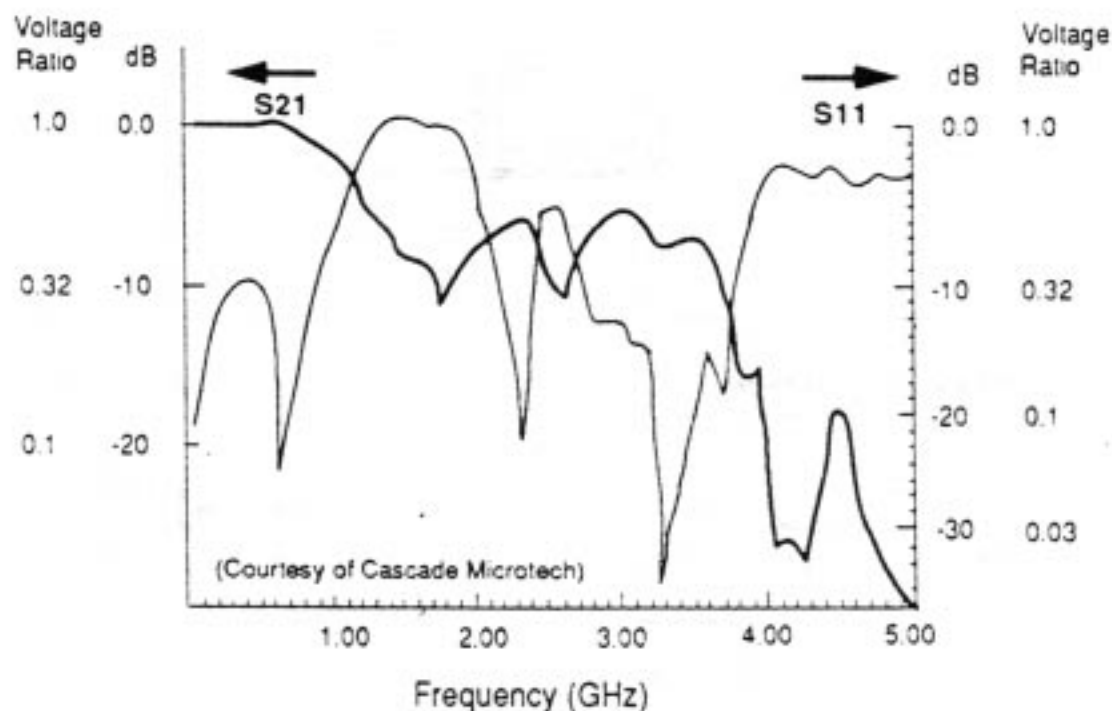


Observations:

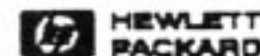- Reflected energy (S_{11}) becomes excessive above 800 MHz
- Bandwidth of package is about 1 GHz (will transmit signals with risetimes as fast as 350 ps without significant distortion assuming interconnect BW = 0.35/tr)



Magnitude and Phase vs Frequency

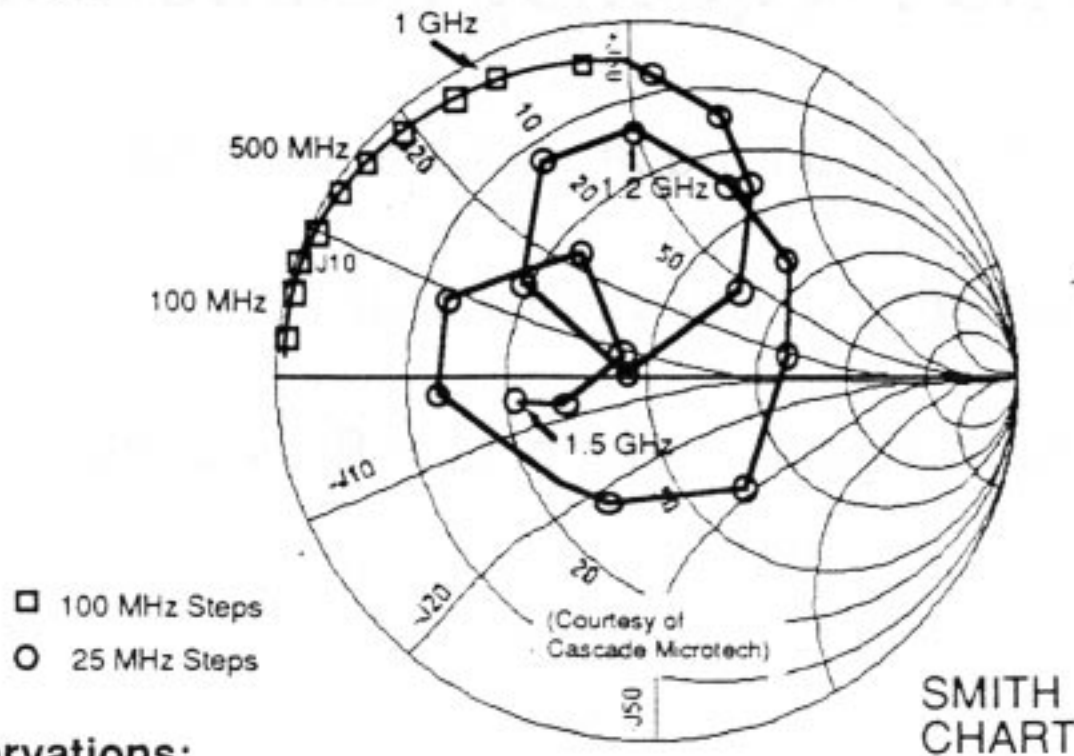


Observations:

- Major effect of package is inductive
- Package becomes lossy above 1 GHz
- Ability to measure package at higher frequencies reveals several resonances and provides insights as to possible sources of high frequency problem






Time and Frequency Relationships

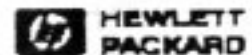- Risetime and Frequency Relationships
- Measurement BW vs Risetime
- Comparing Measurements in Both Domains




Risetime and Frequency Relationships

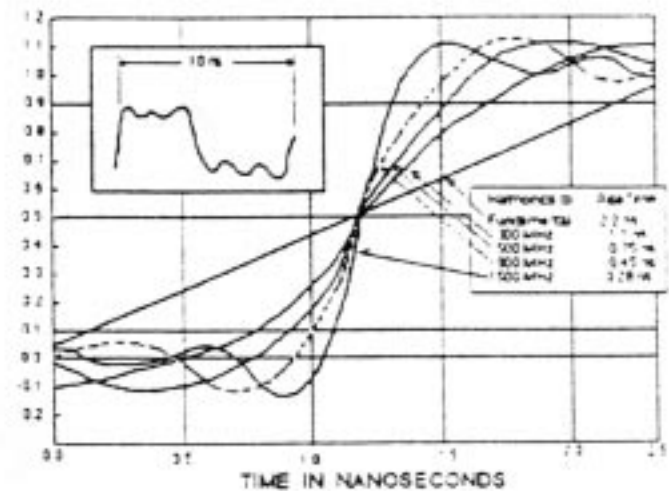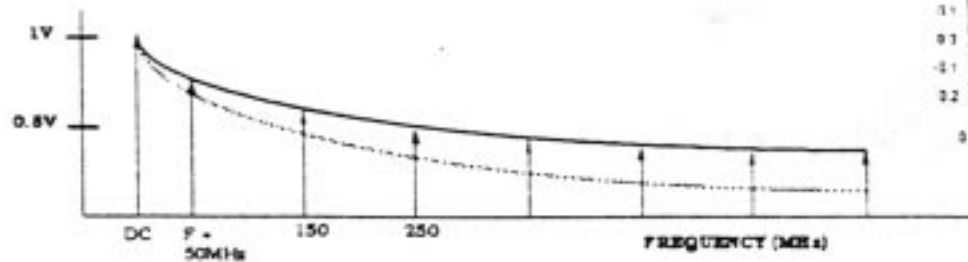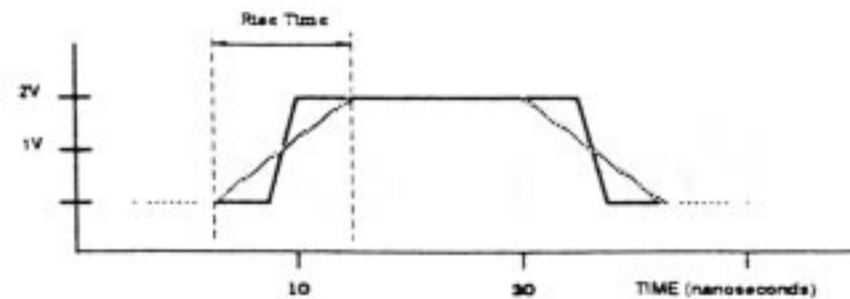

Clock Frequency
=
Bandwidth



Measurement BW vs Risetime

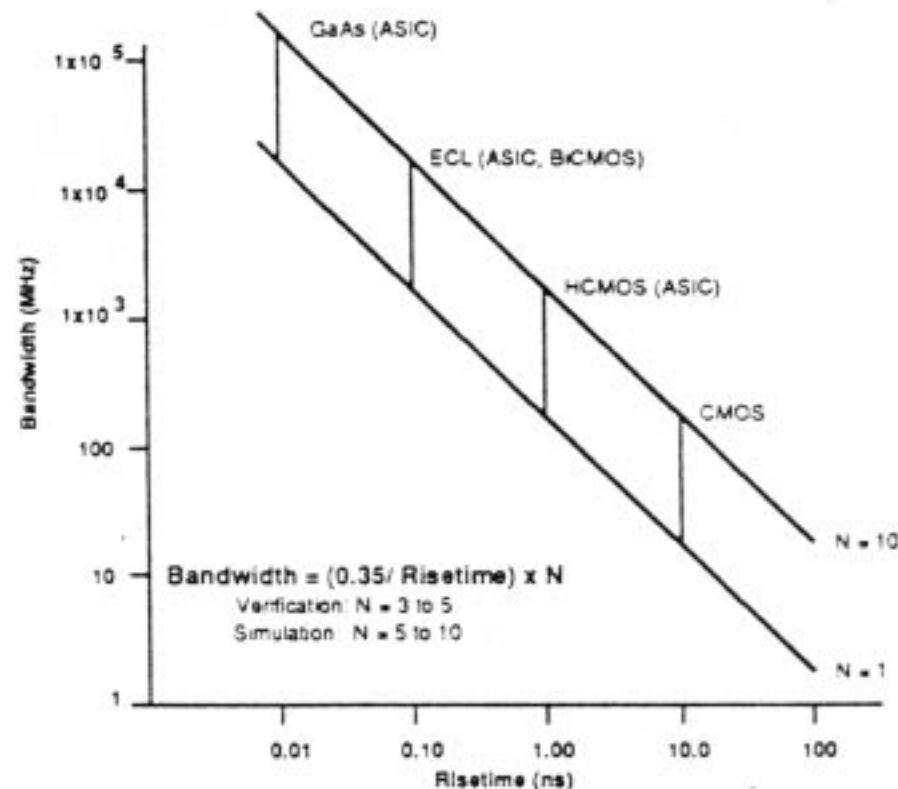


Example: for a pulse risetime of 0.5 ns, what minimum frequency range should be used for hardware verification.

$$BW = (0.35 / 0.5 \times 10^{-9}) \times 5 = 3.5 \times 10^9, \text{ or } 3.5 \text{ GHz}$$




Reflection Parameter Relationships

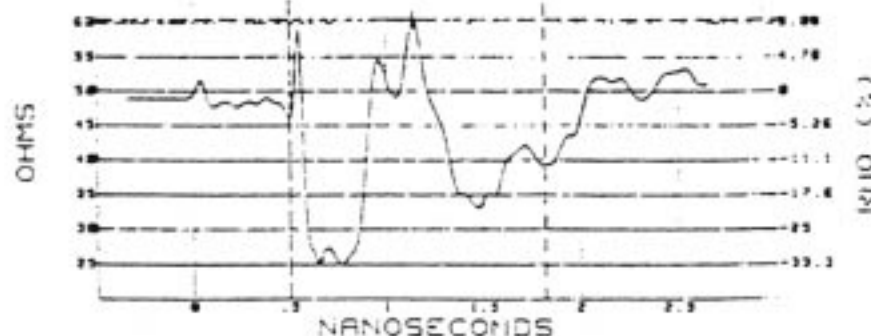TDR 12-12-35 SCOPES4:DEMO.DAT Data Low-Band: 165 MHz TDR: 165 MHz, 400ns 25 May 1998
16-28-12 TDR of 165 MHz PDR, T=400ns 8 Feb 1998



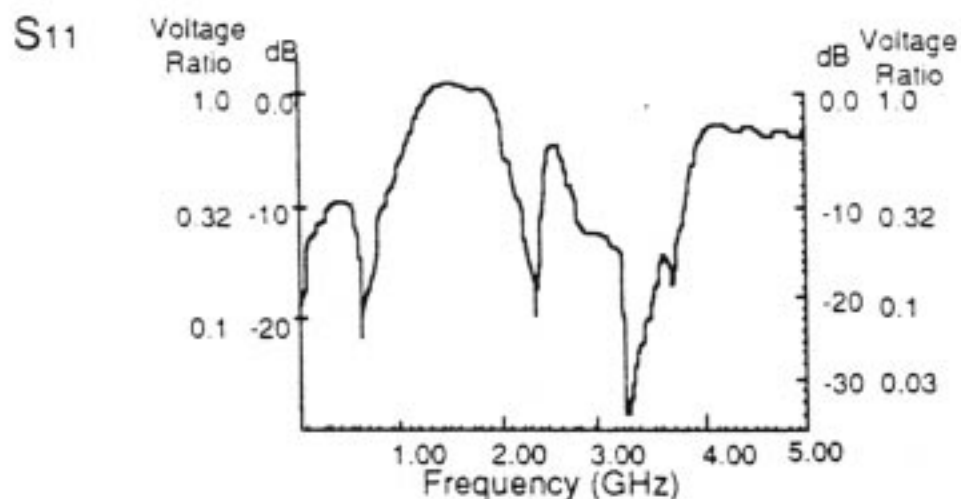Too much impedance variation in the time domain ...




... will appear as reflected energy in the frequency domain



Transmission Parameter Relationships


TDT

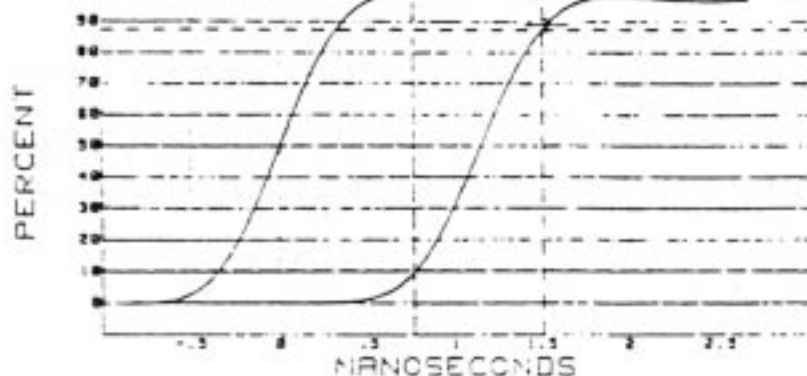18115105 SCOPES+DEMO DATA Name: Lab-Book 165 PCH 1014 165 PCH 7300x 75 75x 1990
18115105 TDT at 165 GHz PCH 7300x 75 75x 1990



Too much risetime degradation in the time domain ...

S21

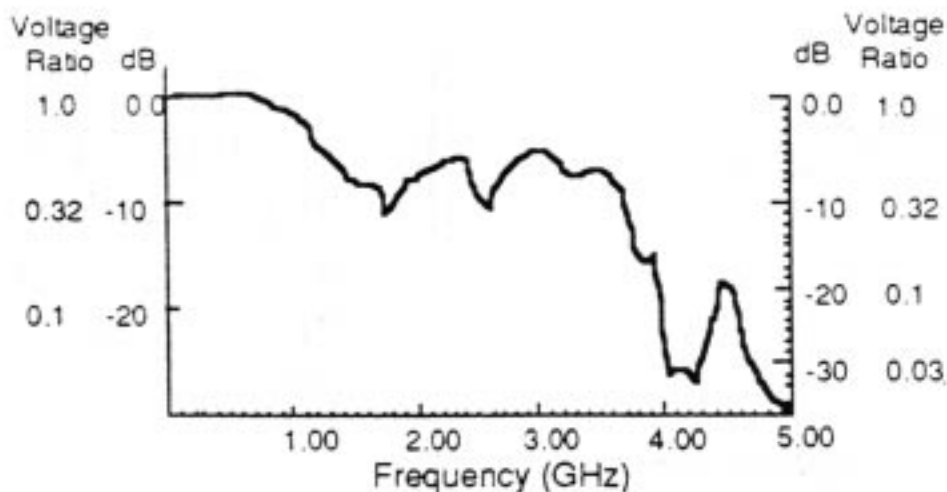

...will appear as inadequate bandwidth in the frequency domain




Crosstalk Parameter Relationship

V21

18 02 17

Graphic of S-parameter K-factor at 200MHz, 100ps

28 Nov 1998

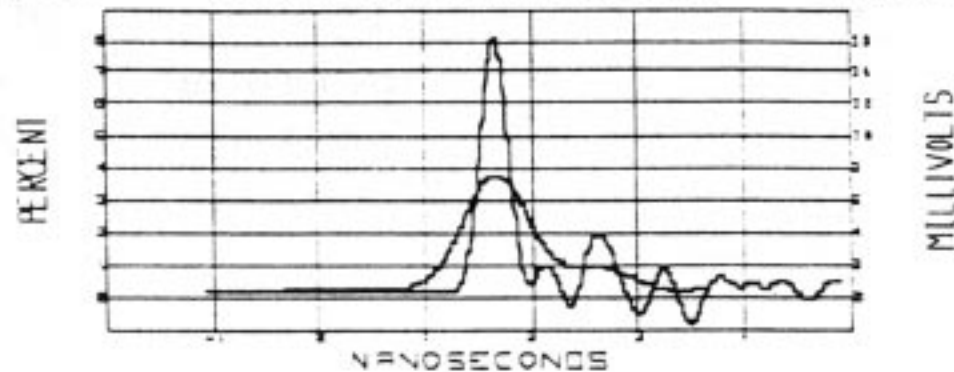

Risetime dependent crosstalk between two traces in the time domain ...

S21

Voltage Ratio

dB

0.32 -10

0.1 -20

0.32 -30

1.00 2.00 3.00 4.00 5.00
Frequency (GHz)



...will appear as decreased isolation at higher frequencies in the frequency domain

Summary

- Measurements vs information
- Instruments vs measurable parameters



Measurements vs Information

- TDR
 - Impedance of elements within package
 - Visual indication of circuit topology
 - Prediction of signal integrity problems due to impedance mismatch
- TDT
 - Indicates propagation delay of package
 - Can view risetime degradation
 - Shows loss in signal amplitude vs time
- S_{11}
 - Shows reflected energy as a function of frequency
 - Can characterize complex loads vs frequency
 - Can see frequency range over which package is mainly inductive or capacitive (Smith Chart)
- S_{21}
 - Gives bandwidth over which package will operate
 - Can calculate risetimes the package will pass
 - Indicates where package resonates (Smith Chart)



Instrumentation vs Measurable Parameters

Instrumentation	Impedance vs. Time	Transmission vs Time	Impedance vs Frequency	Transmission vs Frequency	Magnitude & Phase vs Freq.	Links to MDS
LCZ Meter	No	No	Yes (<40MHz)	Yes (<40MHz)	Yes (<40MHz)	No
TDR O'scope	Yes	Yes	No	No	No	No
Network Analyzer	Yes w/opt	Yes w/opt	Yes	Yes	Yes	Yes

